

Design of an analogic Application Specific Integrated Circuit (ASIC) with open source tools

Benoit Leroux

benoit.leroux@centrale.centralelille.fr

2026-05-05

Contents

1	Introduction	3
2	Typical Design Flow	3
3	Open Source Process Design Kit	3
4	Toolset diving	4
4.1	Schematic	4
4.2	Simulation	4
4.3	Layout and layers geometry	4
4.4	Verification	4
5	IC design elements	4
5.1	Transistors	4
5.1.1	Models	5
5.1.1.1	Switch	5
5.1.1.2	Switch + current source	5
5.1.1.3	Berkeley Short-channel IGFET Model (BSIM)	5
5.1.1.4	Philips Penn State (PSP)	5
5.2	Simple inverter	5
5.2.1	Theory	5
5.2.1.1	Ideal Inverter	5
5.2.1.2	Resistor Inverter	5
5.2.1.3	MOS Inverter	5
5.2.2	Schematic	5
5.2.3	Simulation	6
5.2.4	Layout	7
5.2.5	Post-Layout Checks	9
5.2.5.1	DRC	9
5.2.5.2	LVS	9
5.3	Current Mirror	10
5.3.1	Schematic	10
5.3.2	Simulation	11
5.3.3	Layout	11
5.4	Operationnal Amplifier	12
5.5	Howland pump	13
5.6	Instrumentation Amplifier	13
6	ASIC for a High Temperature Gradient Sensor	13
6.1	Sensor Presentation	13
6.2	Circuit Overview	13
6.2.1	Heating Circuit	13
6.2.2	Current Generator	13
6.2.3	Measurements stage	13
7	Low Cost Manufacturing Model	13
8	Conclusion	13
9	Glossary	13
10	References	15
10.1	Papers and books	15
10.2	Github and links	16

1 Introduction

Integrated Circuit (IC) design in industry is built around tightly controlled, highly optimized flows that prioritize yield, manufacturability, speed to market, and protection of intellectual property. Those priorities shape toolchains, Process Design Kit (PDK), collaboration practices, and business/legal arrangements. While this model is efficient for commercial fabs and large design houses, it creates multiple practical and cultural barriers for academic groups and small laboratories.


The industry model requires signing Non Disclosure Agreement (NDA) to access foundry PDK, which keep device models, layout rules, and parasitic data confidential; this restriction undermines reproducibility and prevents open licensing of designs and layout artifacts. Commercial Electronic Design Automation (EDA) tools and PDK licenses are expensive—often costing thousands of dollars per month for a single tool, placing them out of reach for many university groups and small labs. Production toolchains are complex and heavyweight, demanding intensive training and dedicated engineering support that most students and small research teams cannot sustain. Foundry design constraints and rigorous process rules limit flexibility, making exploratory or unconventional research difficult to pursue within a commercial process.

link to cadence website

Field Programmable Gate Array (FPGA) can mitigate some access and cost issues, but they only address digital designs and do not substitute for analog, mixed-signal, or process-level device experiments that require actual silicon.

The goal of this paper is to present an opinionated, end-to-end design flow that allows an individual to go from idea to fabrication using only tools released under open-source licenses, and to provide additional automation within the chosen toolchain to streamline design, verification, and tapeout for academic and small-lab use.

2 Typical Design Flow

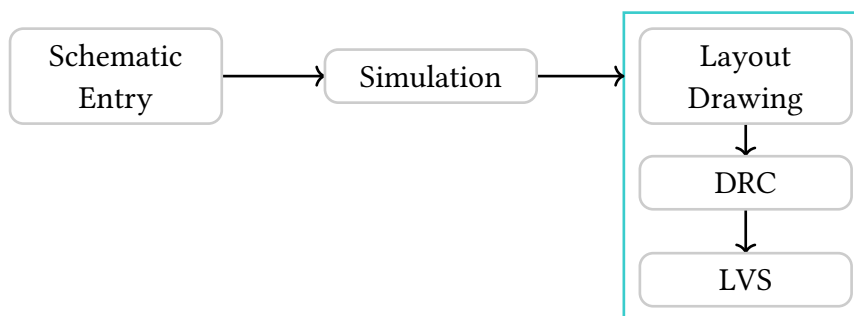

3 Open Source Process Design Kit

- gf180 (US)
- sky130 (US)
- sg13g2 (DE)
- ICPS (JP)

4 Toolset diving

4.1 Schematic

- xschem
- kicad / eSim
- <https://github.com/thesourcerer8/xschem2kicad>

In the rest of this paper we will use xschem for schematic capture.

4.2 Simulation

- ngspice
- xyce
- QUCS-S

4.3 Layout and layers geometry

- Magic
- KLayout
- gdsfactory -> Project seems young and the framework for ihp sg13g2 is a bit misleading (I will try to make my own abstraction of klayout scripting in python)

4.4 Verification

- gds3d

5 IC design elements

5.1 Transistors

Structure:

- MOSFET (MOS)
- BJT
- IGBT

Material:

- germanium
- silicon
- gallium arsenide
- silicon carbide
- alloy silicon-germanium
- allotrop of carbon-graphene

Polarity

- NPN/PNP for BJT
- N-channel/P-channel for BJT

5.1.1 Models

5.1.1.1 Switch

5.1.1.2 Switch + current source

5.1.1.3 BSIM

5.1.1.4 PSP

5.2 Simple inverter

5.2.1 Theory

5.2.1.1 Ideal Inverter

An inverter is a base circuit for most complex logic gates. It is composed of two transistors and its role is to invert the digital signal in entry. When the input is in high state, the output should be low and the inverse should be true when the input is low.

5.2.1.2 Resistor Inverter

5.2.1.3 MOS Inverter


5.2.2 Schematic

In xschem you can load the nmos and pmos components with right click add symbol and add the following components located in `/foss/pdks/ihp-sg13g2/libs.tech/xschem/sg13g2_pr/`

- sg13_lv_pmos
- sg13_lv_nmos

Add as well generic voltage sources for later simulation. Use w to create and connect wires between components. Don't forget to connect the bulk modulus of the nmos channel to the ground and the one of the pmos channel to Vdd.

You should obtain the following result:

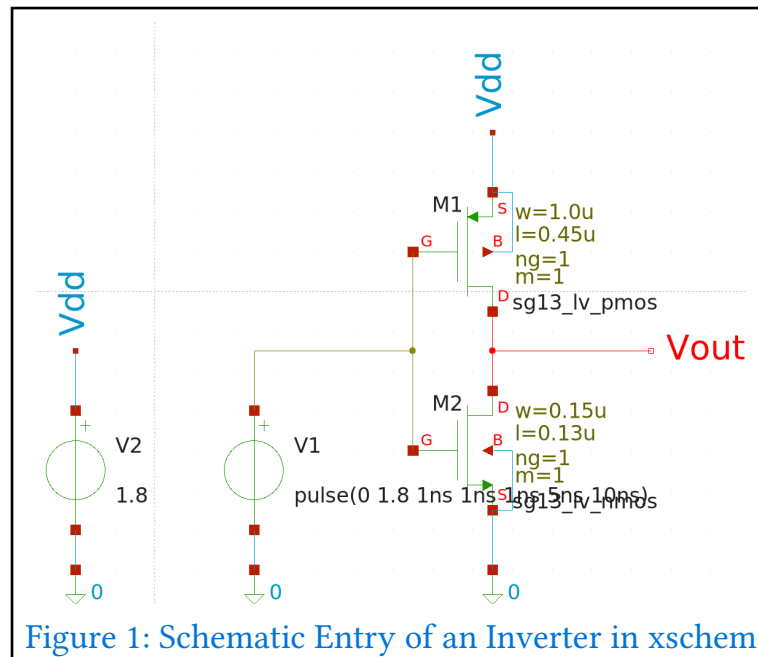

5.2.3 Simulation

In simulation check Use simulator/[schemename] in schematic dir in order to find simulation data more easily.

Code-shown symbols:


```
name=include only_toplevel=false value=".lib cornerMOSlv.lib mos_tt"
name=control only_toplevel=false value=" .control tran 50p 20n *op save all
write inverter-tr.raw dc V1 0 1.8 1m let gain = -deriv(Vout)/12 save all
write inverter-dc-sweep.raw .endc "
```

Make sure the netlist format is spice netlist in Options, Netlist Format / Symbol Format. Then generate the netlist by clicking of the netlist button (you can view the netlist content by pressing shift-A before clicking on netlist).

At this point ngspice will be able to read our netlist to compute the simulation.

Click the simulation button. An interactive prompt will be opened in a new window. You can interact with the computed simulation in this exact window. For example run a plot vout command. You should see a square wave in the ngspice viewer.



I find it usefull to see the result of the simulation directly in our xschem window, so we will add graphs there. Simulation -> Graphs -> Add waveform graphs. You can resize the graph by pressing ctrl plus selecting a corner of the graph then pressing m. Double click on the graph, check auto-load then go load the corresponding .raw file. You can load different signal by typing their name in the editor.

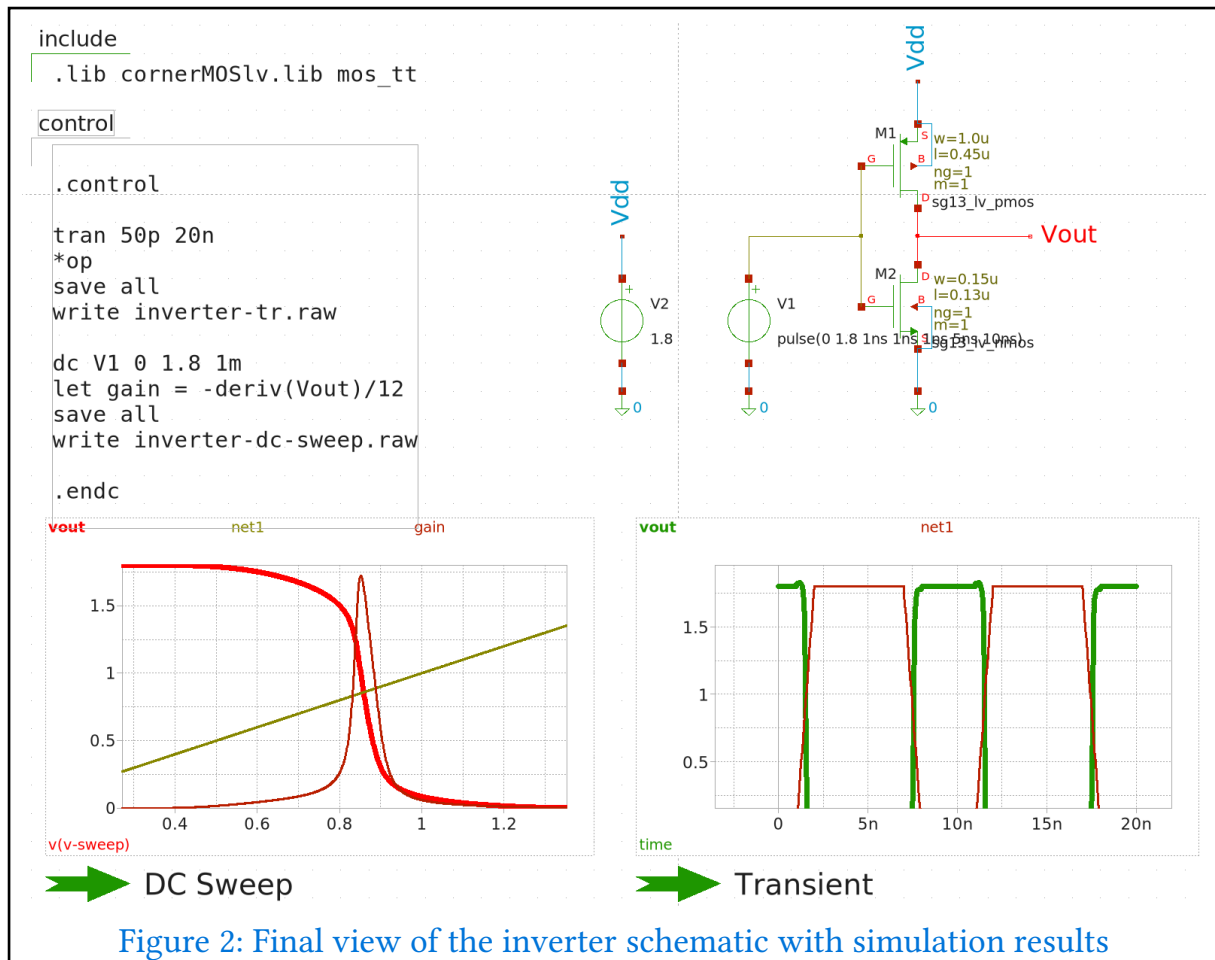

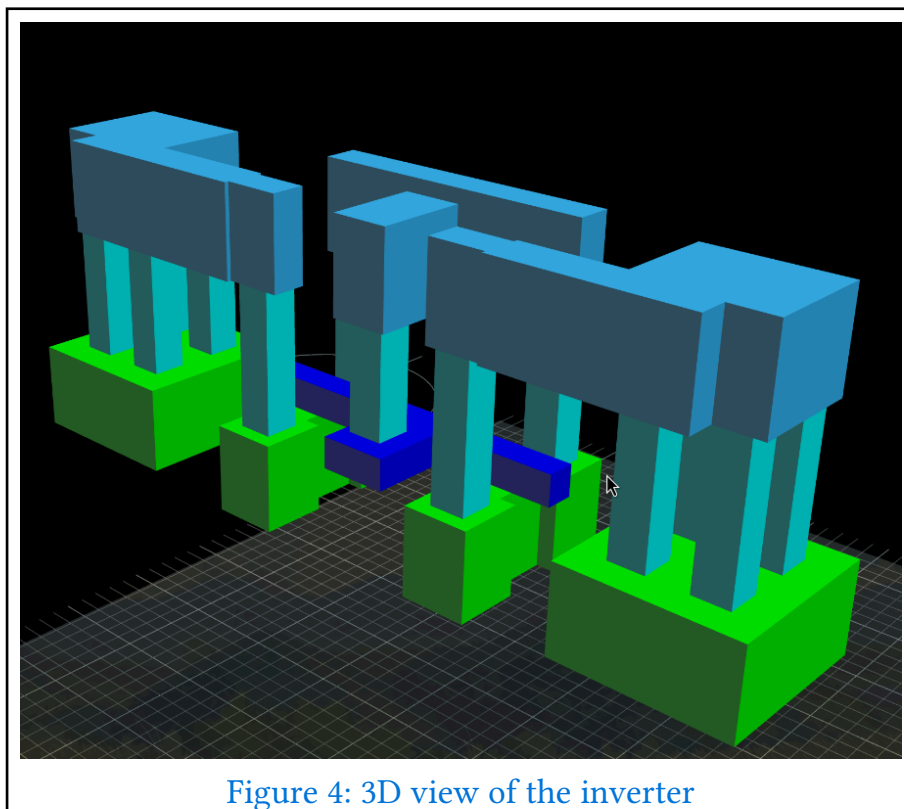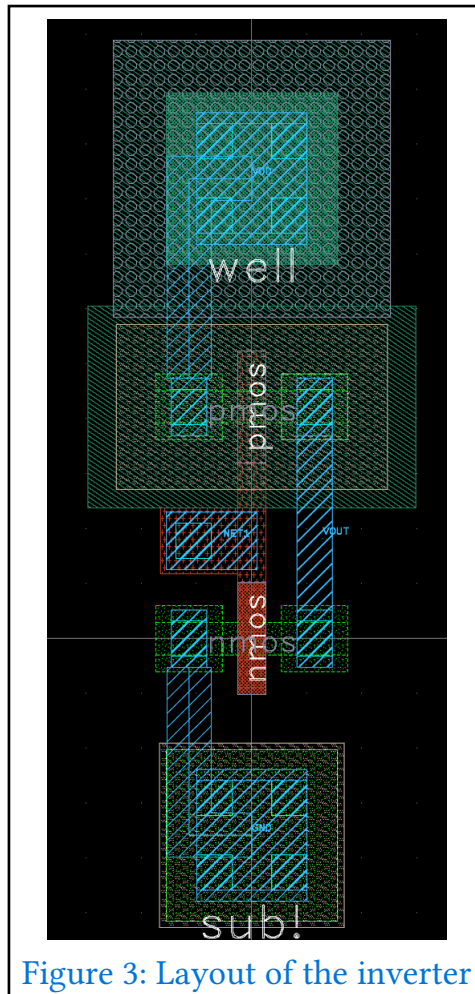5.2.4 Layout

- J'ai essayé avec GDS Layout, mais trop d'erreur lors du routage plus les lms galèrent un peu avec cette librairie
- J'ai essayé avec les macros python de klayout, mais le routage doit être manuel et l'IA galère à faire des routages correct (ils n'ont pas conscience des DRC)


=> Design du layout à la main dans klayout



5.2.5 Post-Layout Checks

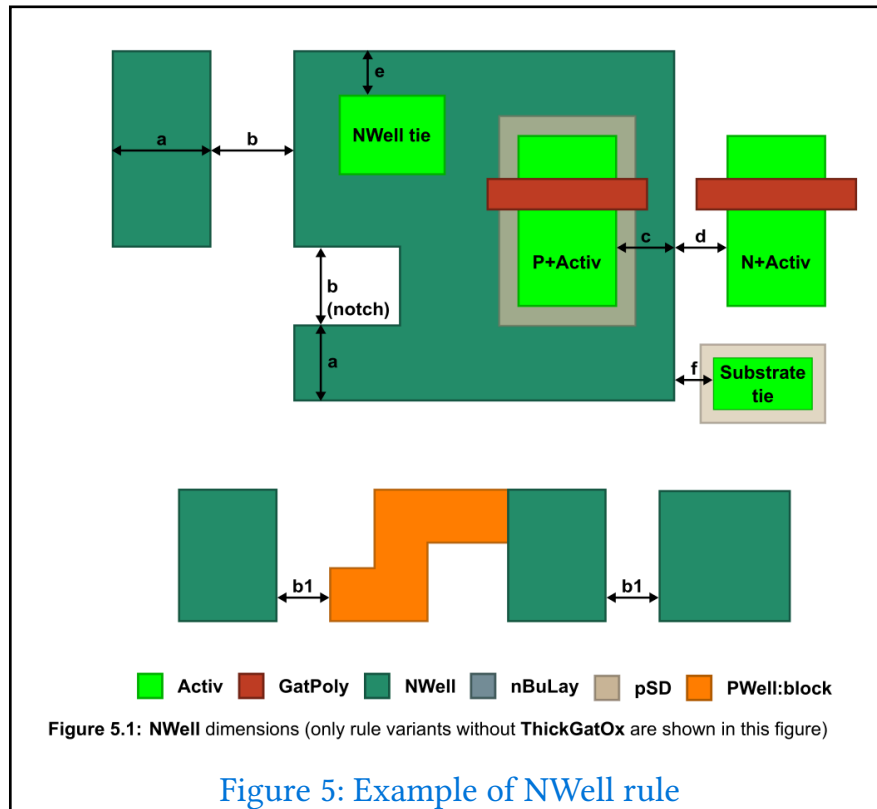5.2.5.1 DRC

Il suffit de lancer le DRC et corriger erreur par erreur. Les différentes erreurs sont expliquées dans le pdf `os_layout_rules` du PDK.



5.2.5.2 LVS

Cette étape permet de comparer la netlist généré à partir de la saisie schématique et la netlist généré à partir du layout, pour vérifier que le layout correspond bien à la schématique saisie.

Dans xschem:

- top level is a .subckt
- disable spicefix attribute

générer la liste et remove les .include et éléments propre à la simulation. s'assurer que le nom après le subckt colle avec le top level element dans klayout (c'est souvent TOP qu'il faut mettre).

Dans klayout LVS option:

- aller chercher la netlist
- cocher:
 - spice comments
 - top level pins
 - verbose

5.3 Current Mirror

A current mirror allows the copy of a current in one active device to another. It will be useful in other designs as it allows to keep the current constant independently of the load while making it controllable.

5.3.1 Schematic

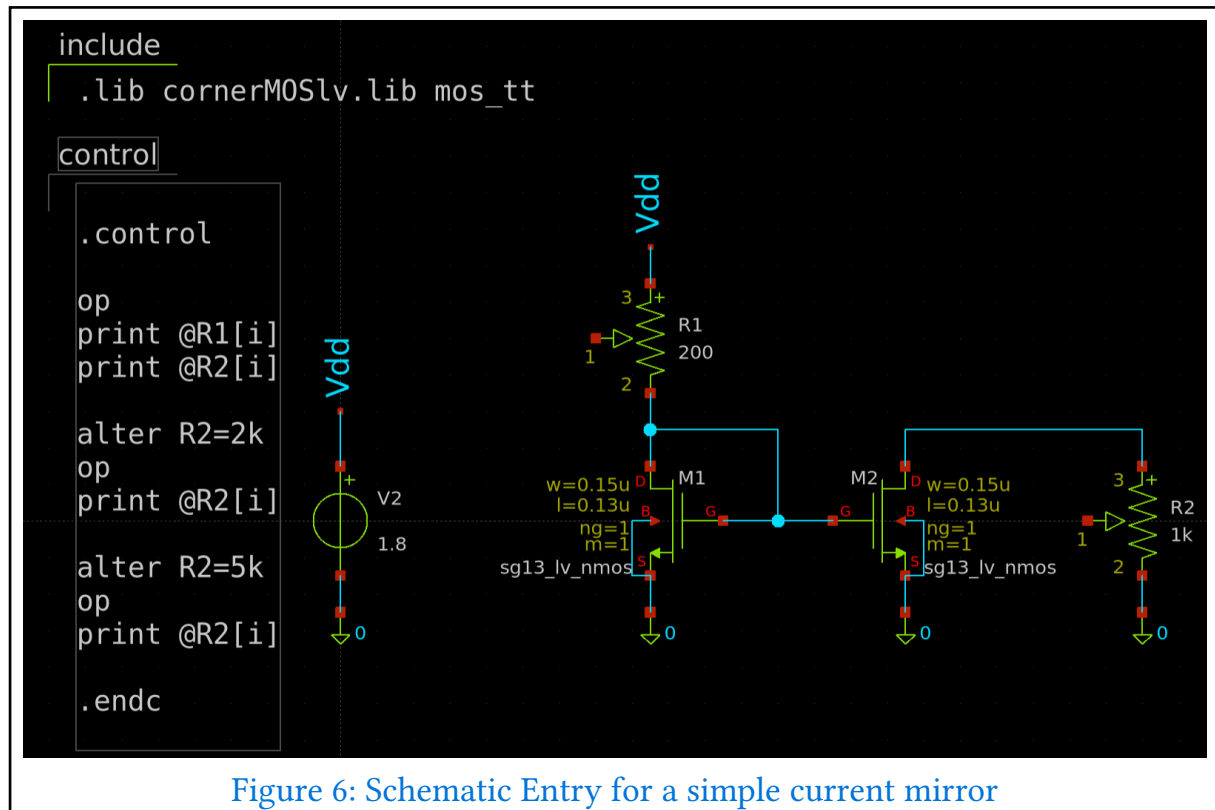


Figure 6: Schematic Entry for a simple current mirror

5.3.2 Simulation

```
Circuit: ** sch_path: /var/home/bleroux/documents/stage_iemn/analog-asic-design/
designs/current_mirror/current_mirror.sch

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Using SPARSE 1.3 as Direct Linear Solver

No. of Data Rows : 1
@r1[i] = 1.508760e-04
@r2[i] = 1.508760e-04
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Using SPARSE 1.3 as Direct Linear Solver

No. of Data Rows : 1
@r1[i] = 1.508760e-04
@r2[i] = 1.491436e-04
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Using SPARSE 1.3 as Direct Linear Solver

No. of Data Rows : 1
@r1[i] = 1.508760e-04
@r2[i] = 3.446018e-05
ngspice 6 -> █
```

Figure 7: Static simulation for the current mirror

5.3.3 Layout

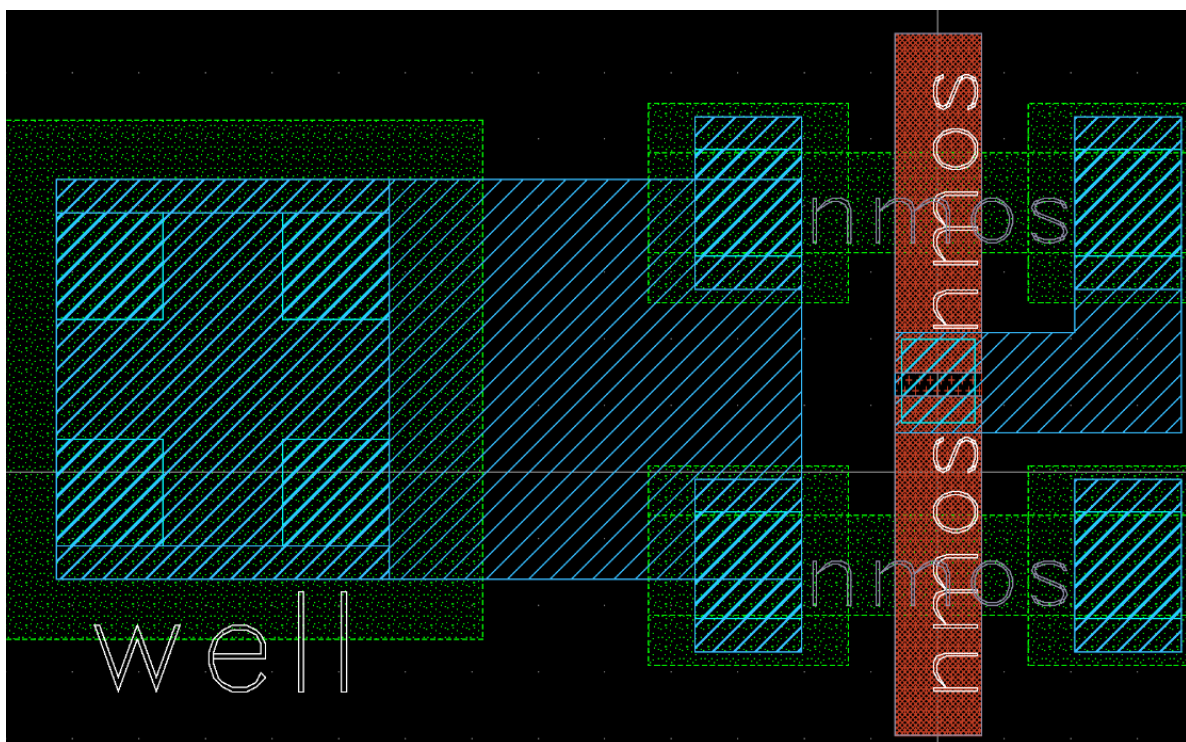


Figure 8: Layout of a current Mirror

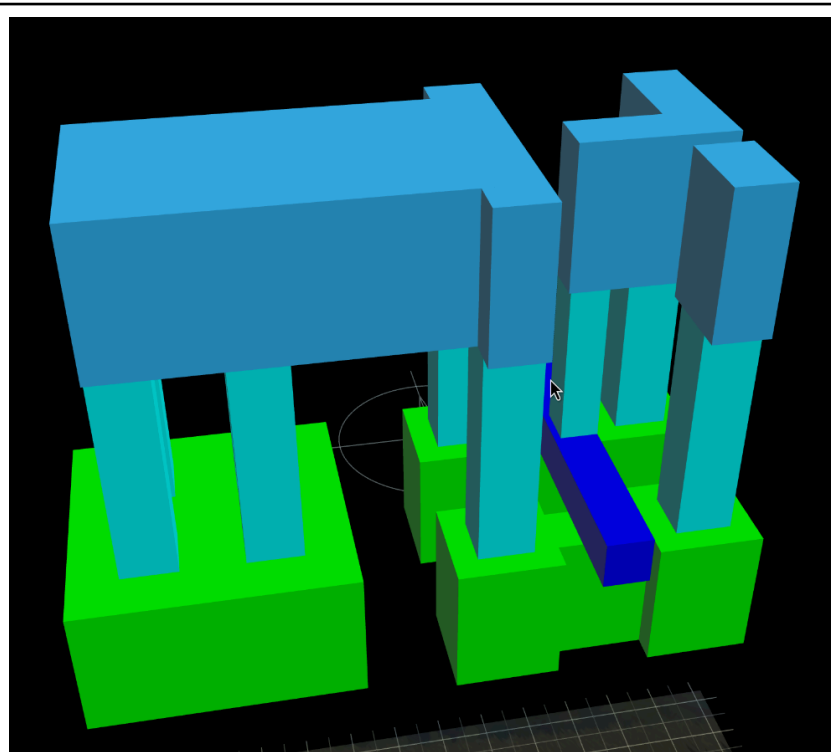


Figure 9: 3D view of the layout from Figure 8

5.4 Operationnal Amplifier

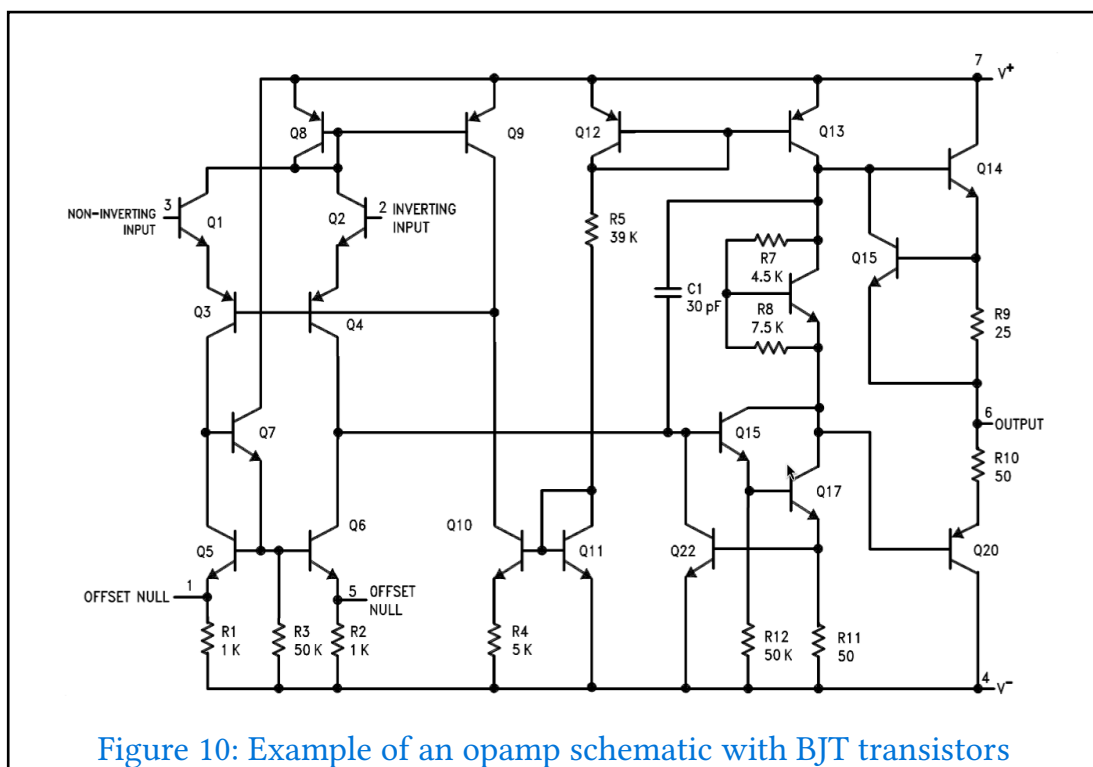


Figure 10: Example of an opamp schematic with BJT transistors

5.5 Howland pump

5.6 Instrumentation Amplifier

6 ASIC for a High Temperature Gradient Sensor

6.1 Sensor Presentation

The sensor is composed of 4 resistors. A heating resistance, a feedback resistance and two measurement resistances. The heating resistance is driven by a closed loop with the feedback resistance to achieve the desired temperature.

6.2 Circuit Overview

The circuit can be decomposed into 3 parts:

- The heating closed loop
- The multiplexer and amplification stage for measurement
- A current generator

6.2.1 Heating Circuit

6.2.2 Current Generator

6.2.3 Measurements stage

7 Low Cost Manufacturing Model

- multi project wafer
- efabless
- tinytapeout

8 Conclusion

9 Glossary

ASIC – Application Specific Integrated Circuit 1, 2, 13

☐

☐

☐

☐

☐

BSIM – Berkeley Short-channel IGFET Model: MOS model 2, 5

☐

☐

- ☐
- ☐
- ☐

CMOS – Complementary Metal Oxyde Semiconductor: Both NMOS and PMOS are fabricated on the same chip.

- ☐
- ☐
- ☐
- ☐
- ☐

EDA – Electronic Design Automation 3

- ☐
- ☐
- ☐
- ☐
- ☐

FPGA – Field Programmable Gate Array 3

- ☐
- ☐
- ☐
- ☐
- ☐

IC – Integrated Circuit 3

- ☐
- ☐
- ☐
- ☐
- ☐

NDA – Non Disclosure Agreement 3

☐☐☐☐☐

PDK – Process Design Kit 3, 3, 3, 9

☐☐☐☐☐

PSP – Philips Penn State: MOS model 2, 5

☐☐☐☐☐

10 References

10.1 Papers and books

- IHP SG13G2 Layout Rules rev 4.0
- Cécile Ghouila-Houri, J. Claudel, J.C. Gerbedoen, Q. Gallas, E. Garnier, et al.. High temperature gradient micro-sensor for wall shear stress and flow direction measurements. Applied Physics Letters, 2016, 109 (241905), 4 p. [10.1063/1.4972402](#). [hal-01432](#)
- Cécile Ghouila-Houri, Abdelkrim Talbi, Romain Viard, Quentin Gallas, Eric Garnier, et al.. MEMS High Temperature Gradient Sensor for Skin-Friction Measurements in Highly Turbulent Flows. IEEE Sensors Journal, 2021, 21 (8), pp.9749-9755. [10.1109/JSEN.2020.2991785](#). [hal-03229029](#)
- Analog (Integrated) Circuit Design - Harald Pretl Johannes Kepler University harald.pretl@jku.at - Michael Koefinger - Simon Dorrer
- Analysis and design of Elementary MOS amplifier stages - Boris Murmann
- CMOS VLSI design A circuit and system perspective - Neil H. E. Weste - David Money Harris

- Sub-Miniature Hot-Wire Anemometry for High Reynolds Number Turbulent Flows - Milad Samie
- FOSS CAD/EDA Tools Supporting The European Open Access PDK Initiative - FOSSDEM 2024

10.2 Github and links

- https://github.com/diegohernando/caravel_fulgor_opamp
- https://tinytapeout.com/chips/tt06/tt_um_dsatzabal_opamp
- <https://github.com/TechBlueprint-V/Two-stage-Op-amp>
- <https://github.com/iic-jku/iic-osic-tools>
- <https://github.com/IHP-GmbH/IHP-Open-PDK>